

Science

Have a look at these circuits.

For the first three, label each section of the circuit with the correct circuit component.

For the last circuit, see if you can re-draw them using the correct scientific symbols.

