

Science

Complete this table by drawing the correct symbol for each component in a circuit.

Remember that there may be two symbols for some of them!

<u>Circuit component</u>	<u>Scientific symbol</u>
Bulb	
Cell	
Battery	
Wire	
Motor	
Buzzer	
Open Switch	
Closed Switch	