

Electricity

WALT: observe and explain the effects of differing voltages in a circuit.

What Difference Does the Volt Make?

	0V	1.5V	3.0V	4.5V
Prediction				
Results				

<u>Bulb</u>	0V	1.5V	3V	4.5V
Prediction				
Results				
<u>Motor</u>	0V	1.5V	3V	4.5V
Prediction				
Results				
<u>Buzzer</u>	0V	1.5V	3V	4.5V
Prediction				
Results				

Conclusion:

From the experiment, I found out. _____
